

Basic Electronics Engineering (Spring 2024)

Resources of PPT:

- ❑ www.google.com
- ❑ Digital Design, 4th Edition
M. Morris Mano and Michael D. Ciletti

Analog Electronics



Reference Book:

1. **R. BOYLESTAD and L. NASHELSKY, “Electronic Devices And Circuit Theory”, Prentice Hall.**
2. **Sedra and Smith, “Microelectronic Circuits”, Oxford University Press**

OPAMP: Operational Amplifier

Basic characteristics:

- high gain differential amplifier
- high input impedance (ideally infinite Z_{in})
- low output impedance (ideally zero Z_{out})

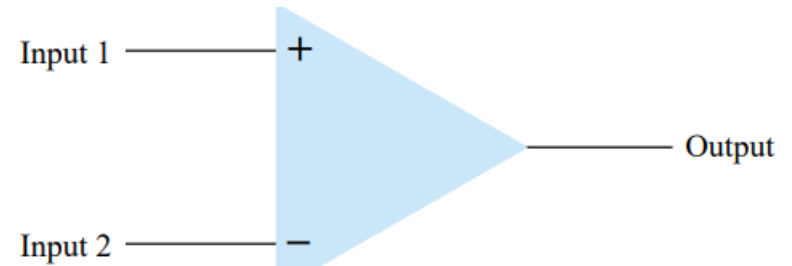


Fig: Basic op-amp.

Single-Ended OPAMP:

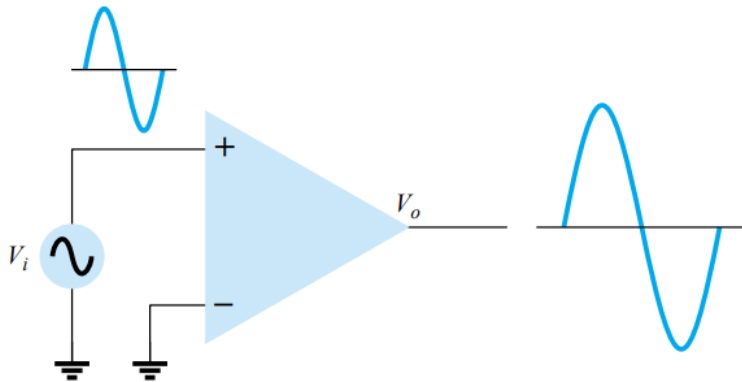


Fig: Input at non-inverting terminal.


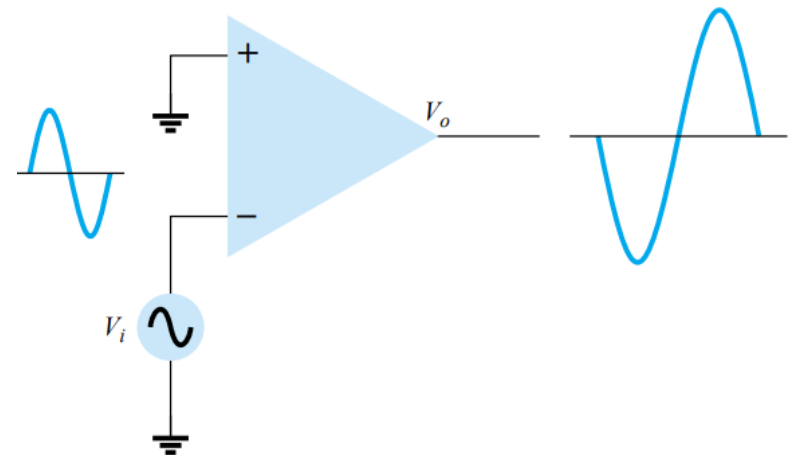
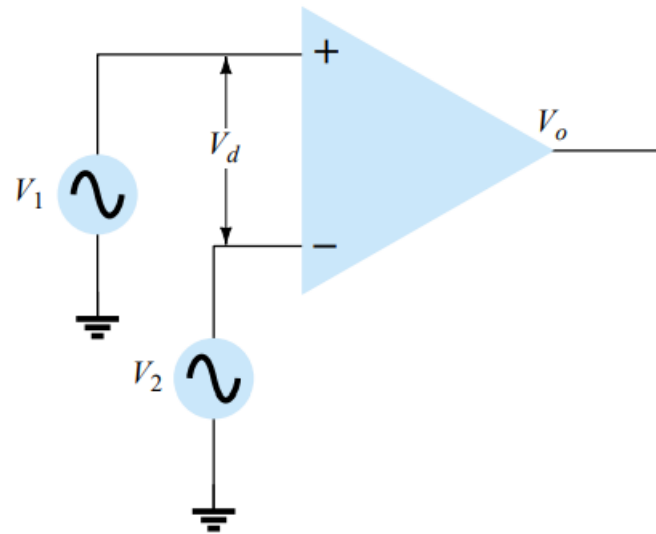


Fig: Input at inverting terminal.



OPAMP: Operational Amplifier

Double-Ended (Differential) Input:

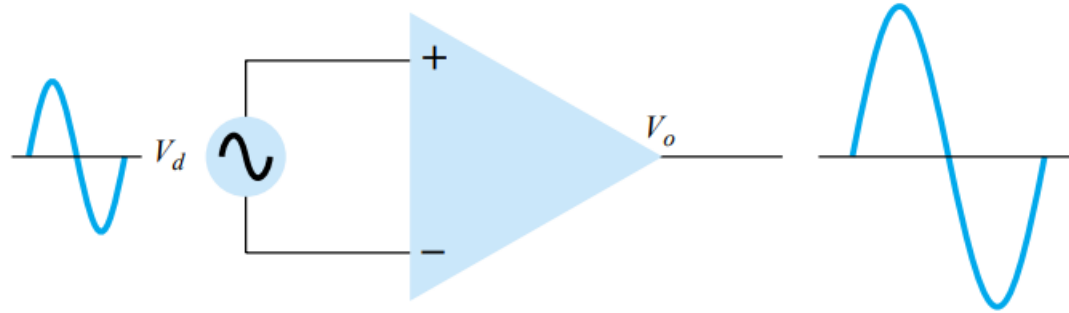

OPAMP: Operational Amplifier

Double-Ended Output:

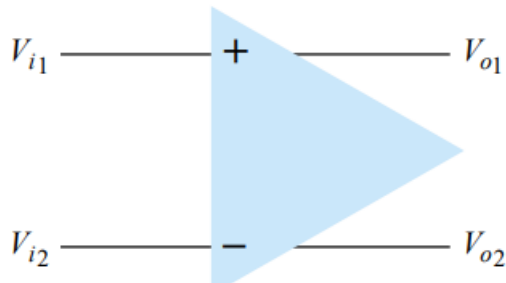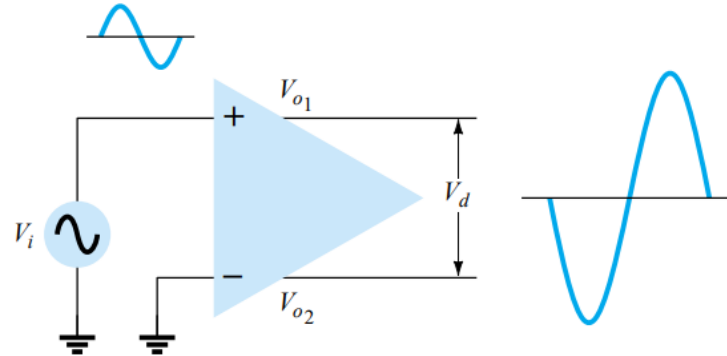

$$V_o = A_d V_d + A_c V_c$$

$$V_c = \frac{1}{2}(V_{i1} + V_{i2})$$

$$V_d = V_{i1} - V_{i2}$$

V_d = difference voltage

V_c = common voltage

A_d = differential gain of the amplifier

A_c = common-mode gain of the amplifier

Common-Mode Rejection Ratio (CMRR):

$$\text{CMRR} = \frac{A_d}{A_c}$$

$$\text{CMRR (log)} = 20 \log_{10} \frac{A_d}{A_c}$$

OPAMP: Operational Amplifier



Determine the output voltage of an op-amp for input voltages of $V_{i_1} = 150 \mu\text{V}$, $V_{i_2} = 140 \mu\text{V}$. The amplifier has a differential gain of $A_d = 4000$ and the value of CMRR is:

- (a) 100.
- (b) 10^5 .

$$V_d = V_{i_1} - V_{i_2} = (150 - 140) \mu\text{V} = 10 \mu\text{V}$$

$$V_c = \frac{1}{2}(V_{i_1} + V_{i_2}) = \frac{150 \mu\text{V} + 140 \mu\text{V}}{2} = 145 \mu\text{V}$$

$$\begin{aligned} V_o &= A_d V_d \left(1 + \frac{1}{\text{CMRR}} \frac{V_c}{V_d} \right) \\ &= (4000)(10 \mu\text{V}) \left(1 + \frac{1}{100} \frac{145 \mu\text{V}}{10 \mu\text{V}} \right) \\ &= 40 \text{ mV}(1.145) = \mathbf{45.8 \text{ mV}} \end{aligned}$$

$$V_o = (4000)(10 \mu\text{V}) \left(1 + \frac{1}{10^5} \frac{145 \mu\text{V}}{10 \mu\text{V}} \right) = 40 \text{ mV}(1.000145) = \mathbf{40.006 \text{ mV}}$$

OPAMP: Operational Amplifier


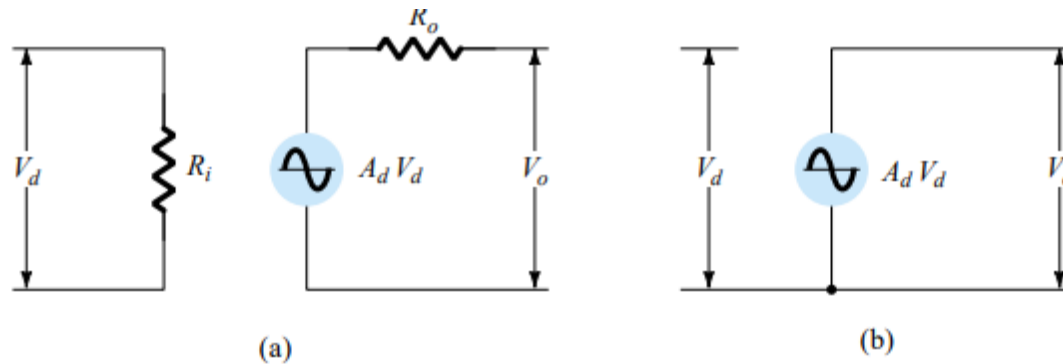
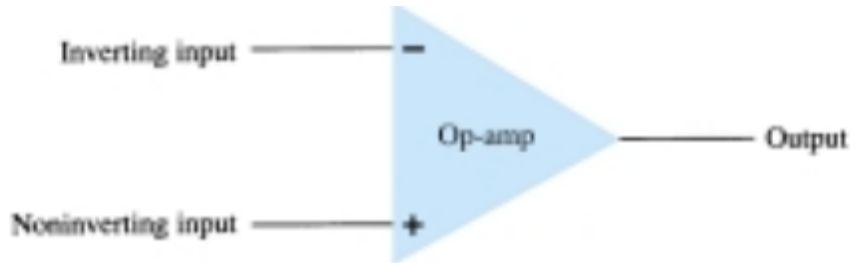



Fig: Ac equivalent of op-amp circuit: (a) practical; (b) ideal.

OPAMP: Operational Amplifier

Inverting Amplifier:

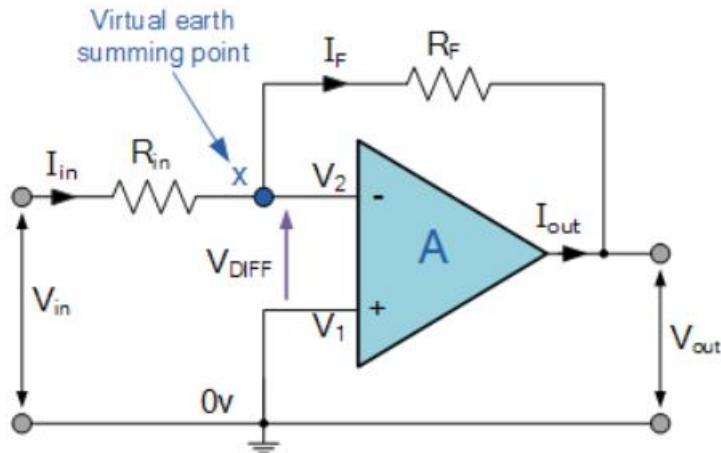

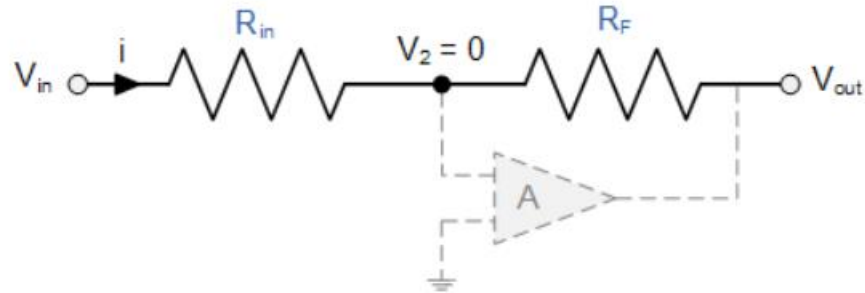- No Current Flows into the Input Terminals
- The Differential Input Voltage is Zero as $V_1 = V_2 = 0$ (Virtual Earth)




$$i = \frac{V_{in} - V_{out}}{R_{in} + R_f} = \frac{V_{in} - V_2}{R_{in}} = \frac{V_2 - V_{out}}{R_f} = \frac{V_{in}}{R_{in}} - \frac{V_2}{R_{in}} = \frac{V_2}{R_f} - \frac{V_{out}}{R_f}$$

$$\frac{V_{in}}{R_{in}} = V_2 \left[\frac{1}{R_{in}} + \frac{1}{R_f} \right] - \frac{V_{out}}{R_f}$$

Closed Loop Gain (A_v) is given as, $\frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}}$


OPAMP: Operational Amplifier

Noninverting Amplifier:

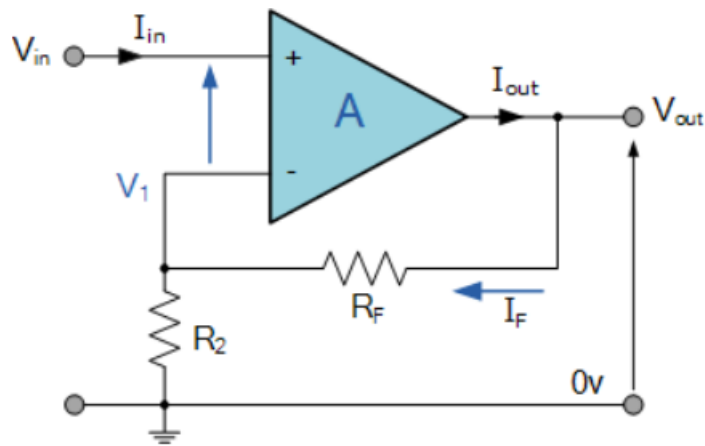

$$V_1 = \frac{R_2}{R_2 + R_F} \times V_{OUT}$$

Ideal Summing Point: $V_1 = V_{IN}$

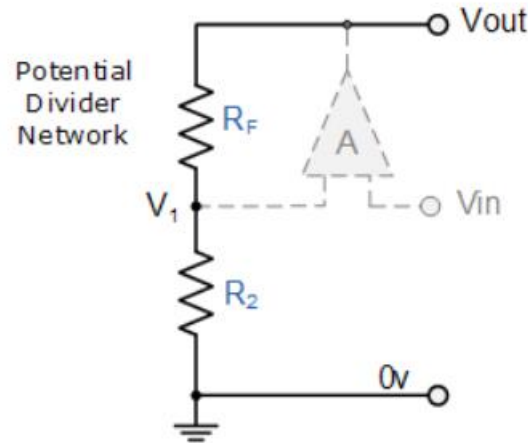


$$\text{Ideal } A_d = \frac{V_o}{V_d} = \frac{V_o}{V_1 - V_2} = \infty$$

So, $V_1 = V_2$

$$A_{(V)} = \frac{V_{OUT}}{V_{IN}} = 1 + \frac{R_F}{R_2}$$


OPAMP: Operational Amplifier

Voltage Follower / Unity Gain Amplifier:

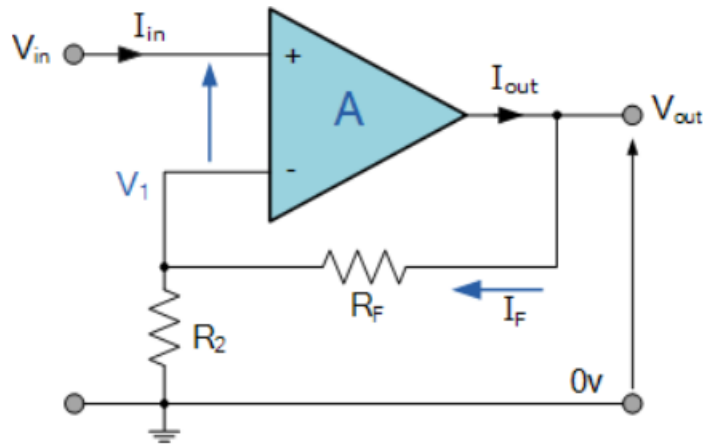



$$R_F = 0$$
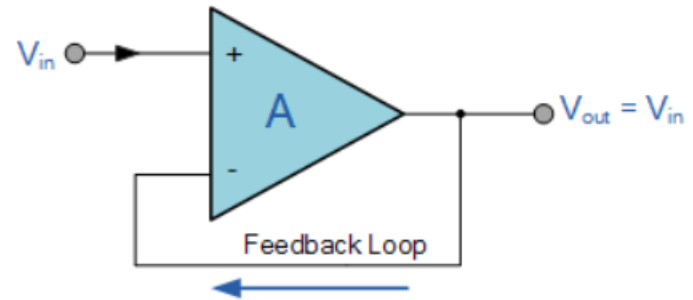
$$A_{(V)} = \frac{V_{OUT}}{V_{IN}} = 1 + \frac{R_F}{R_2} = 1$$



OPAMP: Operational Amplifier

Summing Amplifier:

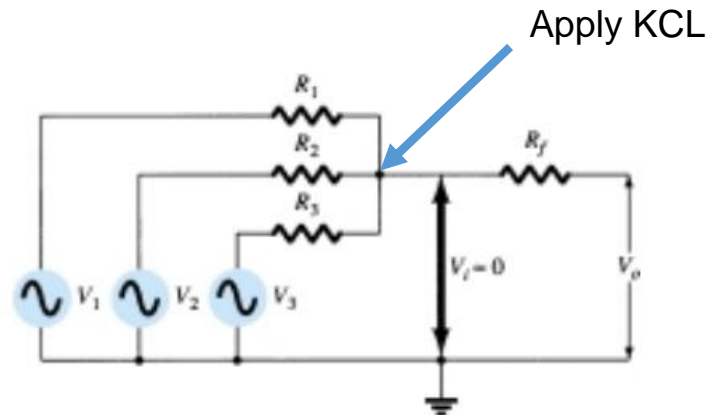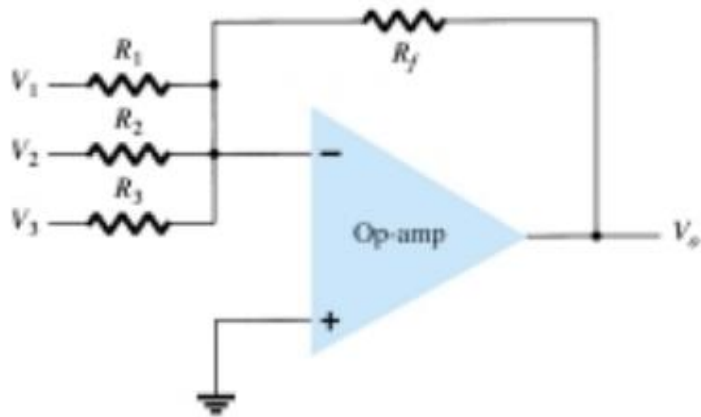

$$V_o = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3\right)$$

OPAMP: Operational Amplifier



Calculate the output voltage of an op-amp summing amplifier for the following sets of voltages and resistors. Use $R_f = 1 \text{ M}\Omega$ in all cases.

(a) $V_1 = +1 \text{ V}$, $V_2 = +2 \text{ V}$, $V_3 = +3 \text{ V}$, $R_1 = 500 \text{ k}\Omega$, $R_2 = 1 \text{ M}\Omega$, $R_3 = 1 \text{ M}\Omega$.

(b) $V_1 = -2 \text{ V}$, $V_2 = +3 \text{ V}$, $V_3 = +1 \text{ V}$, $R_1 = 200 \text{ k}\Omega$, $R_2 = 500 \text{ k}\Omega$, $R_3 = 1 \text{ M}\Omega$.


$$\begin{aligned} \text{(a) } V_o &= - \left[\frac{1000 \text{ k}\Omega}{500 \text{ k}\Omega} (+1 \text{ V}) + \frac{1000 \text{ k}\Omega}{1000 \text{ k}\Omega} (+2 \text{ V}) + \frac{1000 \text{ k}\Omega}{1000 \text{ k}\Omega} (+3 \text{ V}) \right] \\ &= -[2(1 \text{ V}) + 1(2 \text{ V}) + 1(3 \text{ V})] = \mathbf{-7 \text{ V}} \end{aligned}$$

$$\begin{aligned} \text{(b) } V_o &= - \left[\frac{1000 \text{ k}\Omega}{200 \text{ k}\Omega} (-2 \text{ V}) + \frac{1000 \text{ k}\Omega}{500 \text{ k}\Omega} (+3 \text{ V}) + \frac{1000 \text{ k}\Omega}{1000 \text{ k}\Omega} (+1 \text{ V}) \right] \\ &= -[5(-2 \text{ V}) + 2(3 \text{ V}) + 1(1 \text{ V})] = \mathbf{+3 \text{ V}} \end{aligned}$$

OPAMP: Operational Amplifier



Differential Amplifier / Subtractor:

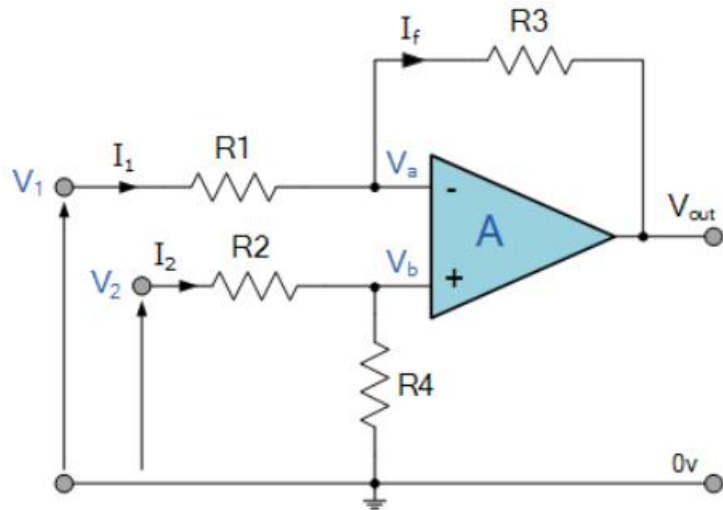

$$I_1 = \frac{V_1 - V_a}{R_1}, \quad I_2 = \frac{V_2 - V_b}{R_2}, \quad I_f = \frac{V_a - (V_{out})}{R_3}$$

Summing point $V_a = V_b$

$$\text{and } V_b = V_2 \left(\frac{R_4}{R_2 + R_4} \right)$$

$$\text{If } V_2 = 0, \text{ then: } V_{out(a)} = -V_1 \left(\frac{R_3}{R_1} \right)$$

$$V_{out} = -V_{out(a)} + V_{out(b)}$$

$$\text{If } V_1 = 0, \text{ then: } V_{out(b)} = V_2 \left(\frac{R_4}{R_2 + R_4} \right) \left(\frac{R_1 + R_3}{R_1} \right)$$

When resistors, $R_1 = R_2$ and $R_3 = R_4$


$$V_{out} = -V_1 \left(\frac{R_3}{R_1} \right) + V_2 \left(\frac{R_4}{R_2 + R_4} \right) \left(\frac{R_1 + R_3}{R_1} \right)$$

$$V_{OUT} = \frac{R_3}{R_1} (V_2 - V_1)$$

OPAMP: Operational Amplifier



Integrator Amplifier:

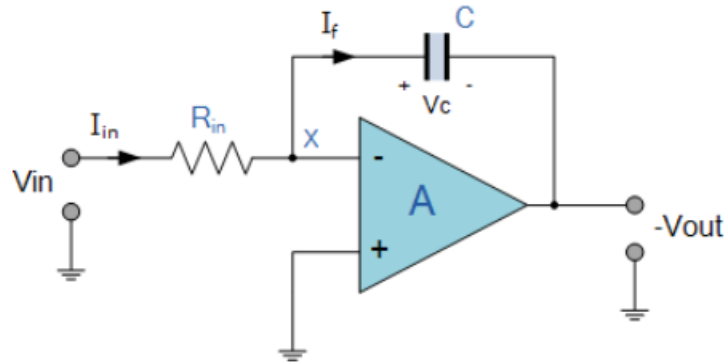

$$V_c = \frac{Q}{C}, \quad V_c = V_x - V_{out} = 0 - V_{out}$$

$$-\frac{dV_{out}}{dt} = \frac{dQ}{Cdt} = \frac{1}{C} \frac{dQ}{dt}$$

$$I_{in} = \frac{V_{in} - 0}{R_{in}} = \frac{V_{in}}{R_{in}}$$

$$I_f = C \frac{dV_{out}}{dt} = C \frac{dQ}{Cdt} = \frac{dQ}{dt} = \frac{dV_{out} \cdot C}{dt}$$


$$I_{in} = I_f = \frac{V_{in}}{R_{in}} = \frac{dV_{out} \cdot C}{dt}$$

$$V_{out} = -\frac{1}{R_{in} \cdot C} \int_0^t V_{in} dt = -\int_0^t V_{in} \frac{dt}{R_{in} \cdot C}$$

OPAMP: Operational Amplifier



Differentiator Amplifier:

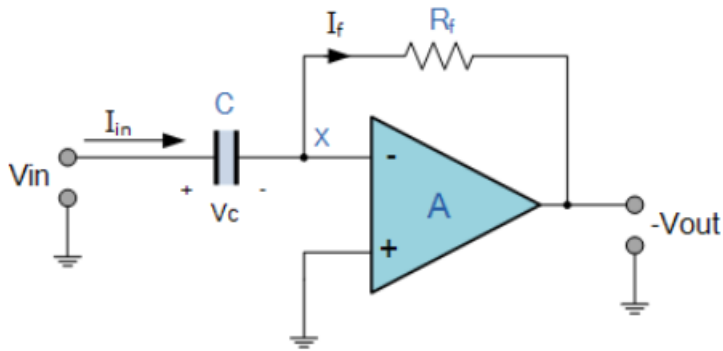

$$I_{IN} = I_F \text{ and } I_F = -\frac{V_{OUT}}{R_F}$$

$$Q = C \times V_{IN}$$

$$\frac{dQ}{dt} = C \frac{dV_{IN}}{dt}$$

$$I_{IN} = C \frac{dV_{IN}}{dt} = I_F$$


$$-\frac{V_{OUT}}{R_F} = C \frac{dV_{IN}}{dt}$$

$$V_{OUT} = -R_F C \frac{dV_{IN}}{dt}$$

OPAMP: Operational Amplifier



Logarithmic Amplifier:

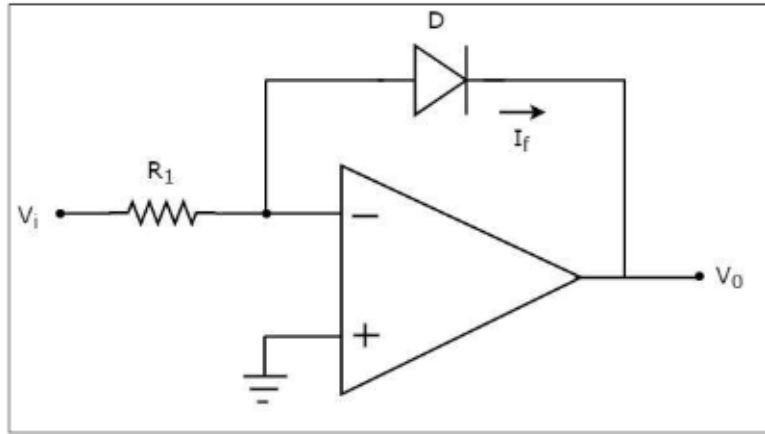

$$0 - V_i/R_1 + I_f = 0$$

$$I_f = V_i/R_1$$

When the diode is forward biased

$$I_f = I_s e^{(V_i/nV_T)}$$

$$0 - V_f - V_o = 0$$

$$V_f = -V_o$$

$$I_f = I_s e^{(-V_o/nV_T)}$$

$$V_i/R_1 = I_s e^{(-V_o/nV_T)}$$

$$V_i/R_1 I_s = e^{(-V_o/nV_T)}$$

$$\ln(V_i/R_1 I_s) = -V_o/nV_T$$

$$V_o = -nV_T \ln(V_i/R_1 I_s)$$

Where,

I_s is the saturation current of the diode,

V_f is the voltage drop across diode, when it is in forward bias,


V_T is the diode's thermal equivalent voltage.

Source: <https://ae-iitr.vlabs.ac.in/exp/log-antilog-amplifier/theory.html#:~:text=A%20logarithmic%20amplifier%20is%20an,connected%20to%20its%20inverting%20terminal.>

OPAMP: Operational Amplifier



Anti-Logarithmic Amplifier

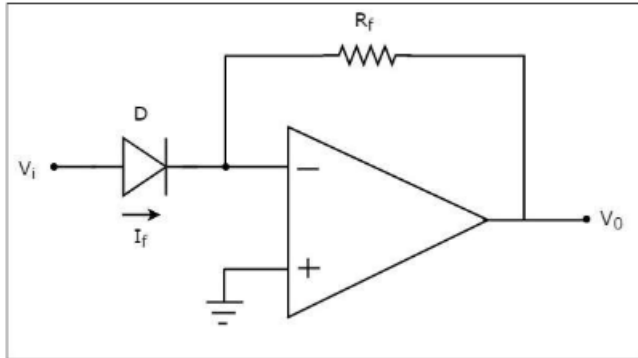

$$-I_f + 0 - V_o/R_f = 0$$

$$V_o = -I_f \cdot R_f$$

$$I_f = I_s e^{(V_f/nV_T)}$$

$$V_o = -R_f I_s e^{(V_f/nV_T)}$$

$$V_i - V_f = 0$$

$$V_i = V_f$$


$$V_o = -R_f I_s e^{(V_i/nV_T)}$$

Source: <https://ae-iitr.vlabs.ac.in/exp/log-antilog-amplifier/theory.html#:~:text=A%20logarithmic%20amplifier%20is%20an,connected%20to%20its%20inverting%20terminal.>

OPAMP: Operational Amplifier



OP-AMP PARAMETERS:

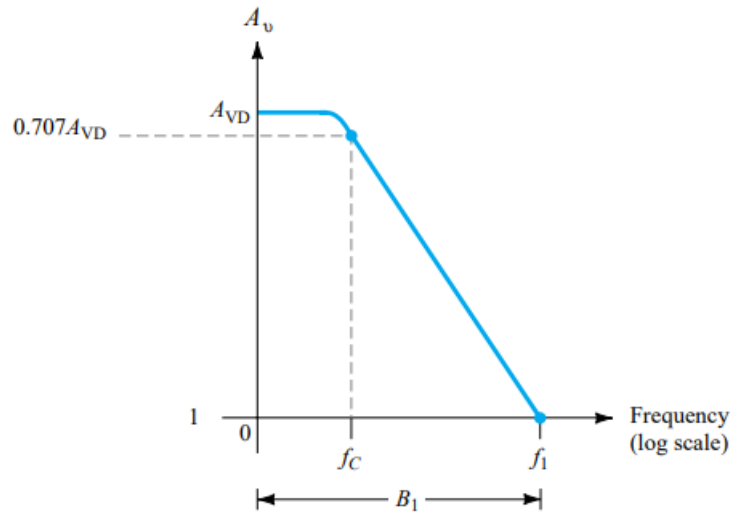

Cutoff frequency (f_c): The frequency at which differential gain of the OPAMP becomes 0.707 times the maximum differential voltage gain.

Unity-gain bandwidth (B_1): The frequency band where differential voltage gain value becomes 1.

$$f_1 = A_{VD} f_c$$

Slew rate (SR): Maximum rate at which amplifier output can change

$$SR = \frac{\Delta V_o}{\Delta t}$$

OPAMP: Operational Amplifier



For an op-amp having a slew rate of $SR = 2 \text{ V}/\mu\text{s}$, what is the maximum closed-loop voltage gain that can be used when the input signal varies by 0.5 V in $10 \mu\text{s}$?

Solution

Since $V_o = A_{CL}V_i$, we can use

$$\frac{\Delta V_o}{\Delta t} = A_{CL} \frac{\Delta V_i}{\Delta t}$$

from which we get

$$A_{CL} = \frac{\Delta V_o / \Delta t}{\Delta V_i / \Delta t} = \frac{SR}{\Delta V_i / \Delta t} = \frac{2 \text{ V}/\mu\text{s}}{0.5 \text{ V}/10 \mu\text{s}} = \mathbf{40}$$

Any closed-loop voltage gain of magnitude greater than 40 would drive the output at a rate greater than the slew rate allows, so the maximum closed-loop gain is 40.

OPAMP: Operational Amplifier



Maximum Signal Frequency

The maximum frequency that an op-amp may operate at depends on both the bandwidth (BW) and slew rate (SR) parameters of the op-amp. For a sinusoidal signal of general form

$$v_o = K \sin(2\pi ft)$$

the maximum voltage rate of change can be shown to be

$$\text{signal maximum rate of change} = 2\pi fK \quad \text{V/s}$$

To prevent distortion at the output, the rate of change must also be less than the slew rate, that is,

$$2\pi fK \leq \text{SR}$$

$$\omega K \leq \text{SR}$$


$$\begin{aligned} f &\leq \frac{\text{SR}}{2\pi K} && \text{Hz} \\ \omega &\leq \frac{\text{SR}}{K} && \text{rad/s} \end{aligned}$$

Additionally, the maximum frequency, f , is also limited by the unity-gain bandwidth.

OPAMP: Operational Amplifier



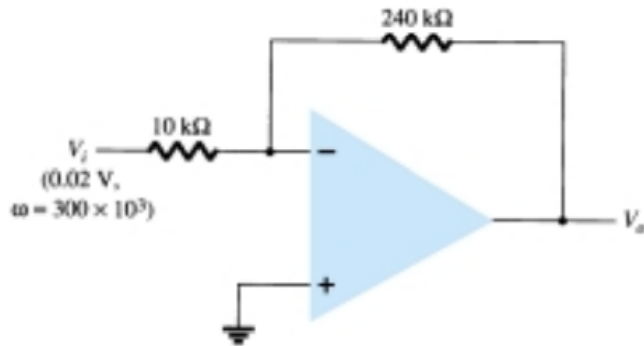For the signal and circuit of Fig. 14.29, determine the maximum frequency that may be used. Op-amp slew rate is $SR = 0.5 \text{ V}/\mu\text{s}$.



Solution

For a gain of magnitude

$$A_{CL} = \left| \frac{R_f}{R_1} \right| = \frac{240 \text{ k}\Omega}{10 \text{ k}\Omega} = 24$$

the output voltage provides

$$K = A_{CL} V_i = 24(0.02 \text{ V}) = 0.48 \text{ V}$$

$$\omega \leq \frac{SR}{K} = \frac{0.5 \text{ V}/\mu\text{s}}{0.48 \text{ V}} = 1.1 \times 10^6 \text{ rad/s}$$

Since the signal's frequency, $\omega = 300 \times 10^3 \text{ rad/s}$, is less than the maximum value determined above, no output distortion will result.