

Basic Electronics Engineering (Spring 2024)

Resources of PPT:

- ❑ www.google.com
- ❑ Digital Design, 4th Edition
M. Morris Mano and Michael D. Ciletti


Analog Electronics



Reference Book:


1. **R. BOYLESTAD and L. NASHELSKY, “Electronic Devices And Circuit Theory”, Prentice Hall.**
2. **Sedra and Smith, “Microelectronic Circuits”, Oxford University Press**

AND/OR Gate Using pn-junction diode

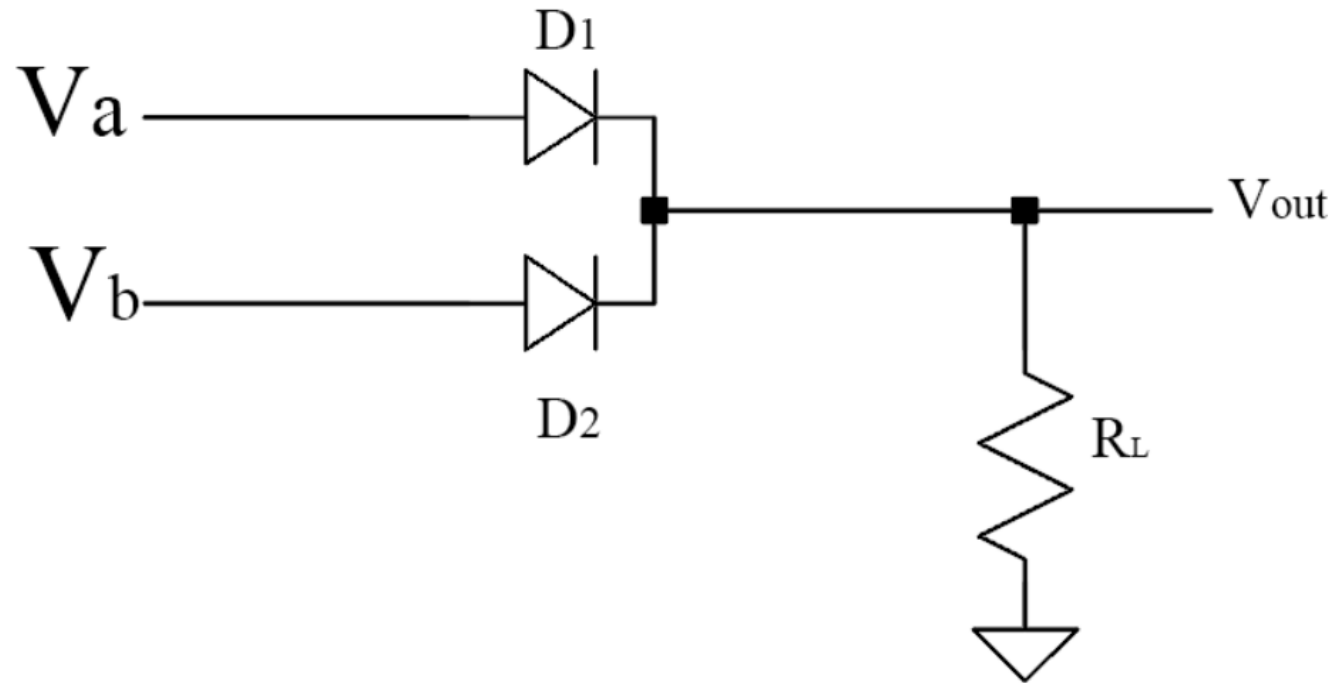



V_a	V_b	V_{out}
LOW	LOW	LOW
LOW	HIGH	HIGH
HIGH	LOW	HIGH
HIGH	HIGH	HIGH

AND/OR Gate Using pn-junction diode

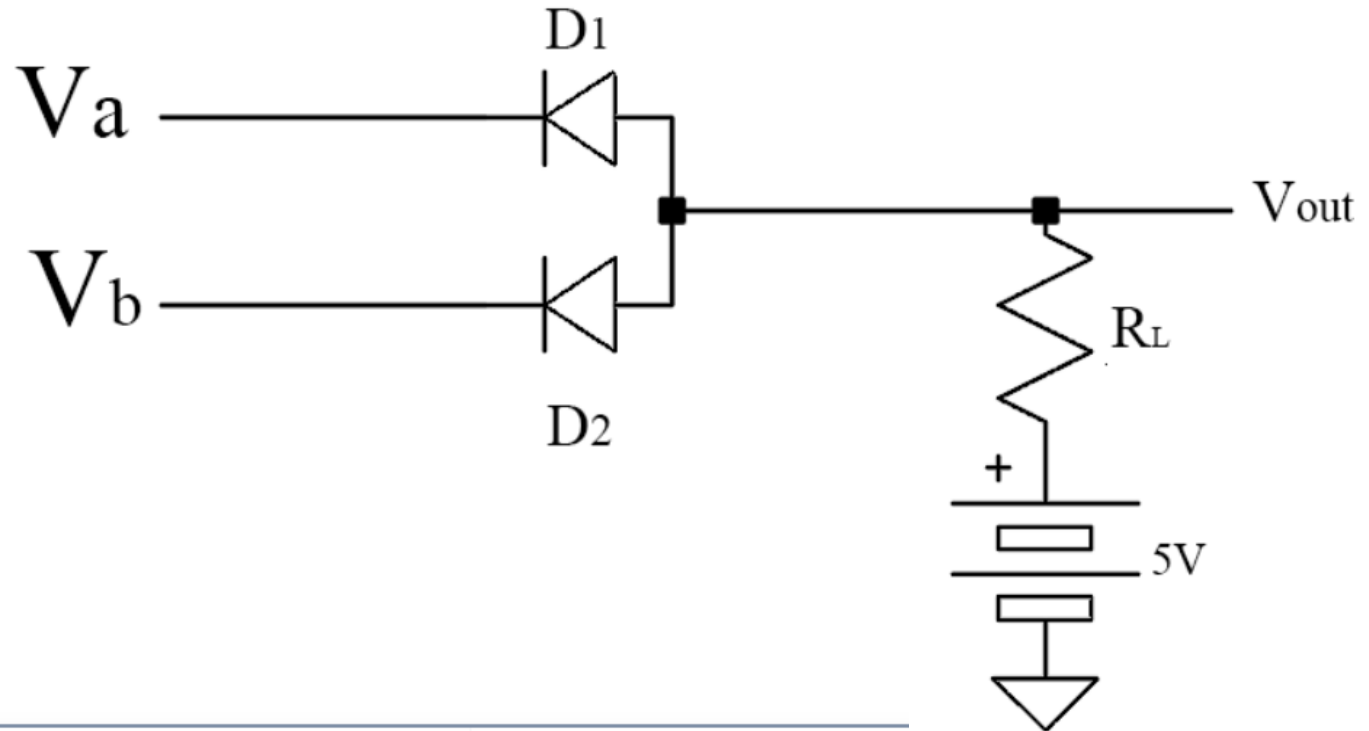



V_a	V_b	V_{out}
LOW	LOW	LOW
LOW	HIGH	LOW
HIGH	LOW	LOW
HIGH	HIGH	HIGH

Ideal Half-wave Rectifier

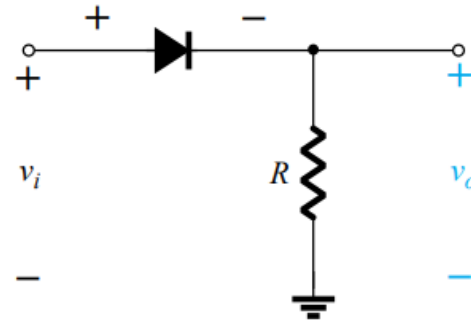
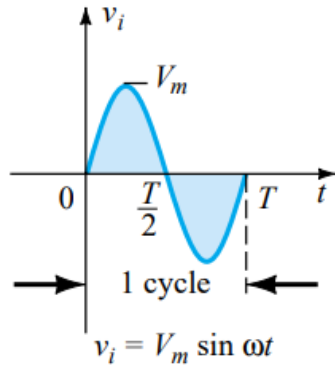


$$v_{dc} = \frac{1}{T} \int_0^T v_o(t) dt$$

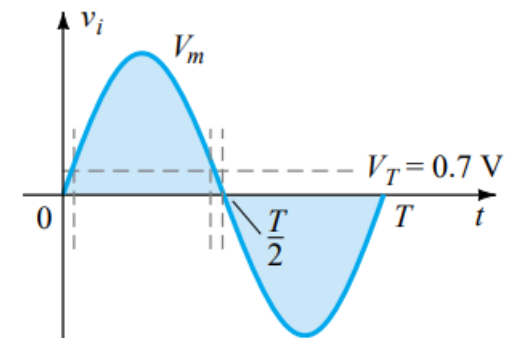
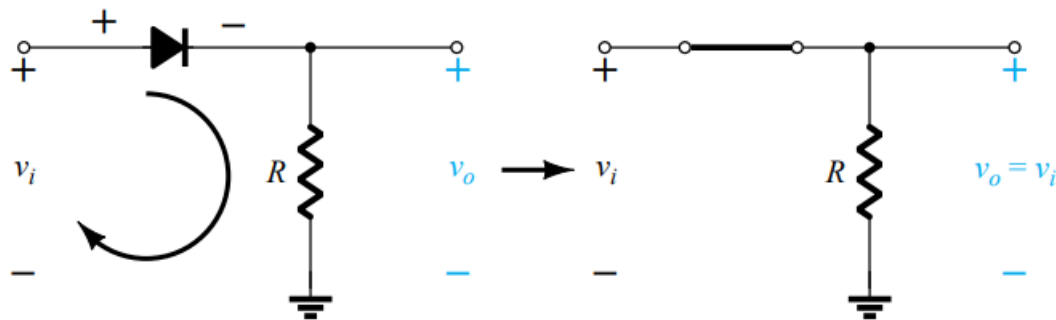
$$V_{dc} = 0.318 V_m \quad \text{half-wave}$$



Non-ideal Half-wave Rectifier

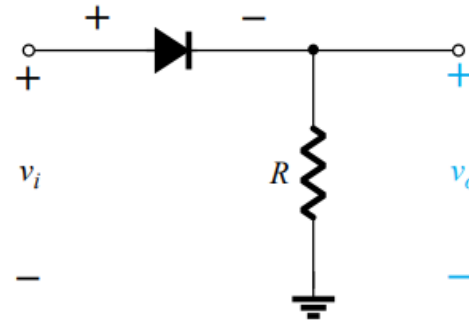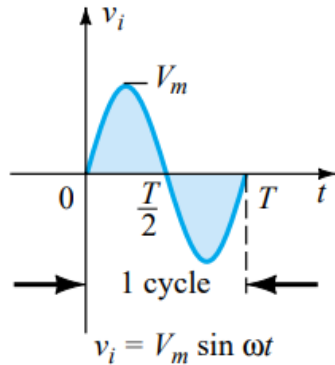

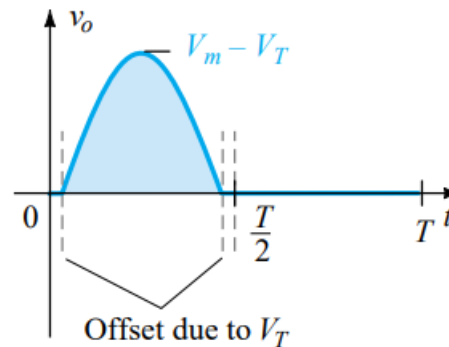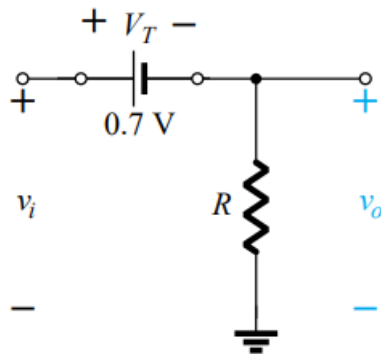
$$v_{dc} = \frac{1}{T} \int_0^T v_o(t) dt$$






$$V_{dc} \cong 0.318(V_m - V_T)$$

pn-junction diode rectifier

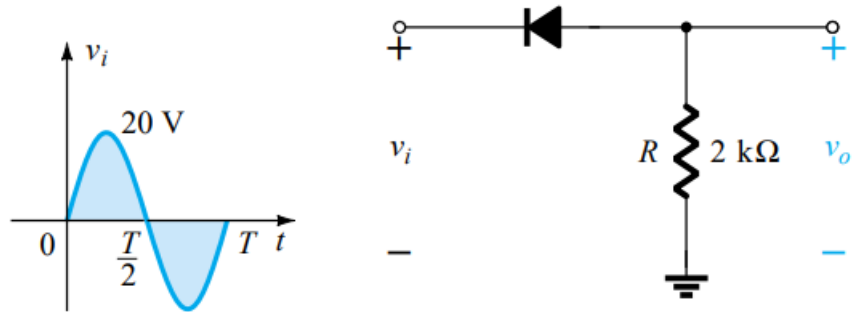

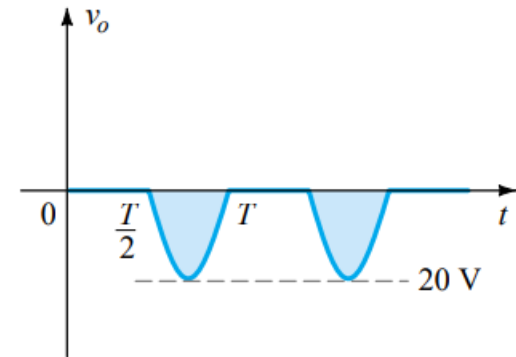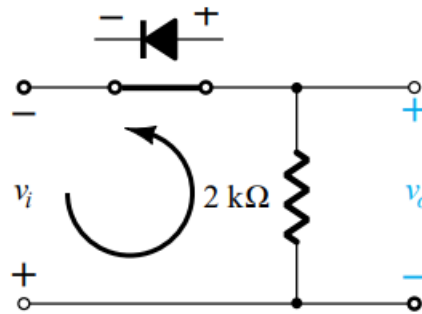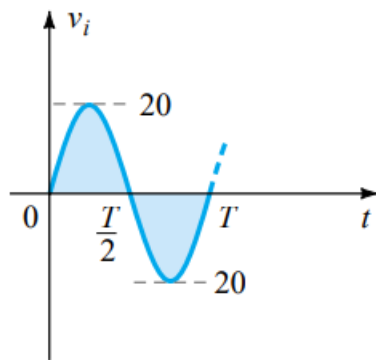- Sketch the output v_o and determine the dc level of the output for the network.
- Repeat part (a) if the ideal diode is replaced by a silicon diode.
- Repeat parts (a) and (b) if v_m is increased to 200 V



$$V_{dc} = -0.318V_m = -0.318(20 \text{ V}) = -6.36 \text{ V}$$

pn-junction diode rectifier



(b) Using a silicon diode, the output has the appearance of Fig. 2.50 and

$$V_{dc} \cong -0.318(V_m - 0.7 \text{ V}) = -0.318(19.3 \text{ V}) \cong \mathbf{-6.14 \text{ V}}$$

The resulting drop in dc level is 0.22 V or about 3.5%.

(c) Eq. (2.7): $V_{dc} = -0.318V_m = -0.318(200 \text{ V}) = \mathbf{-63.6 \text{ V}}$

Eq. (2.8): $V_{dc} = -0.318(V_m - V_T) = -0.318(200 \text{ V} - 0.7 \text{ V})$
 $= -(0.318)(199.3 \text{ V}) = \mathbf{-63.38 \text{ V}}$

which is a difference that can certainly be ignored for most applications. For part c the offset and drop in amplitude due to V_T would not be discernible on a typical oscilloscope if the full pattern is displayed.



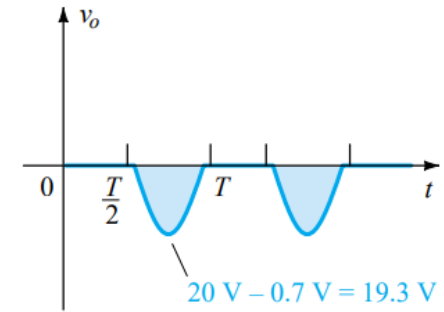
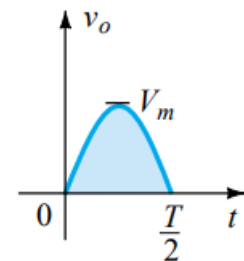
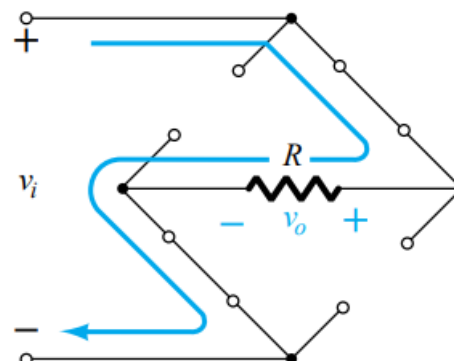
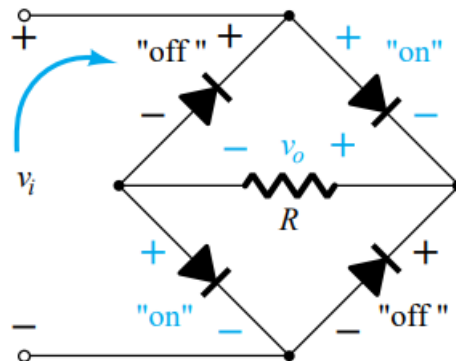
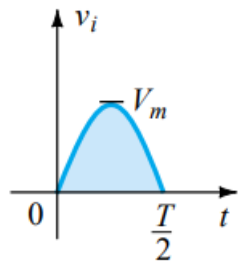
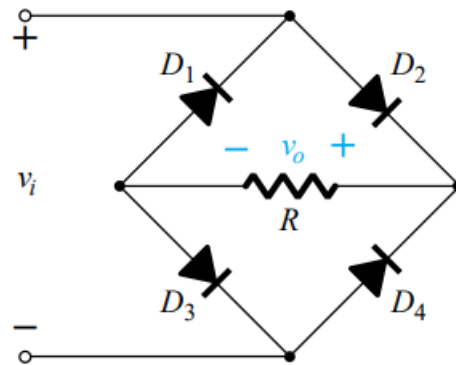
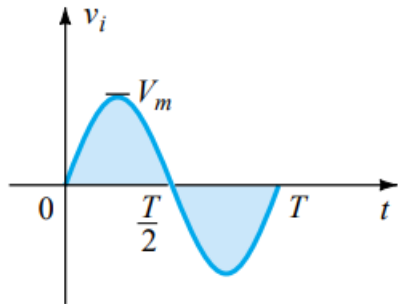
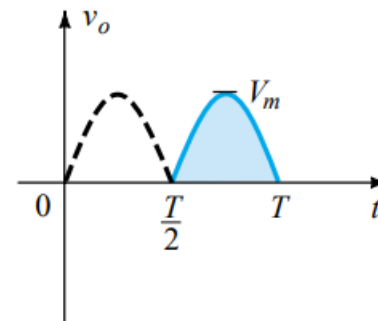
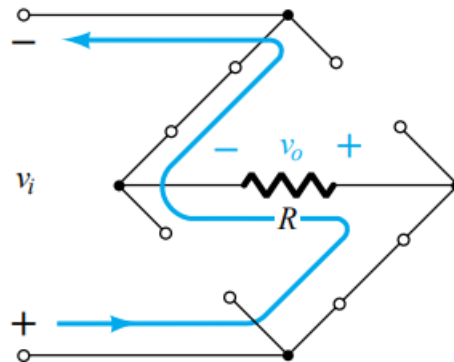
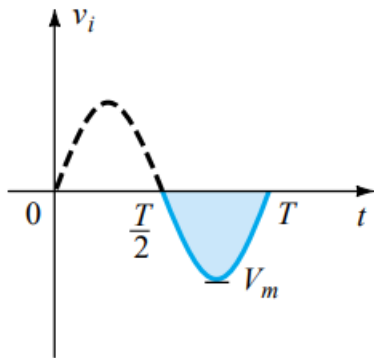


Figure 2.50 Effect of V_T on output of Fig. 2.49.



Full-wave Bridge rectifier

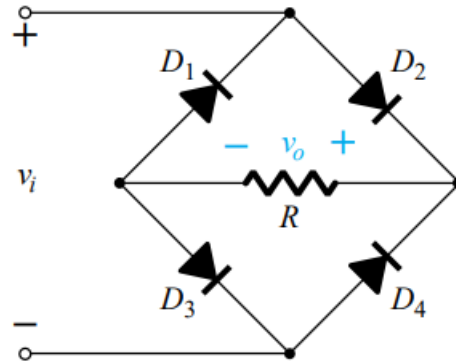



Full-wave Bridge rectifier

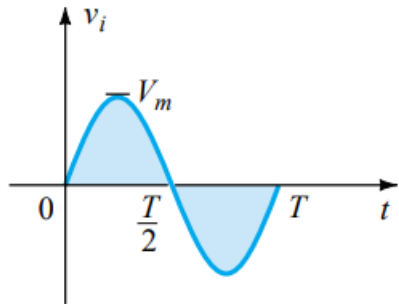

Full-wave Bridge rectifier








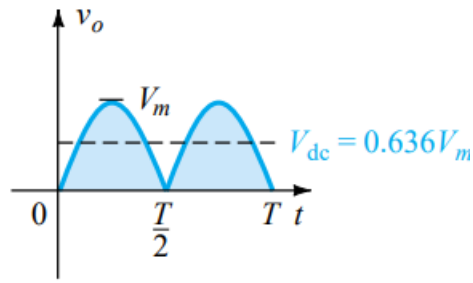
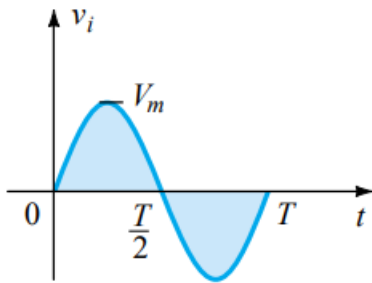

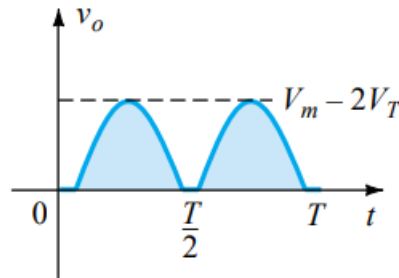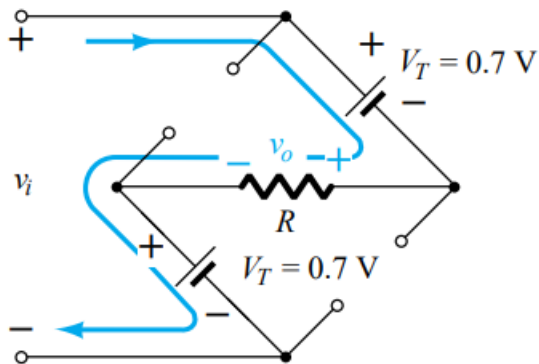
$$V_{dc} = 0.636 V_m \quad \text{full-wave}$$







$$V_{dc} \cong 0.636(V_m - 2V_T)$$



Clipper

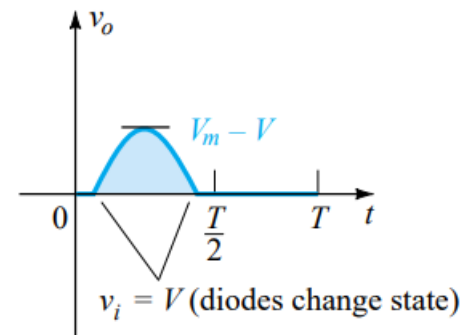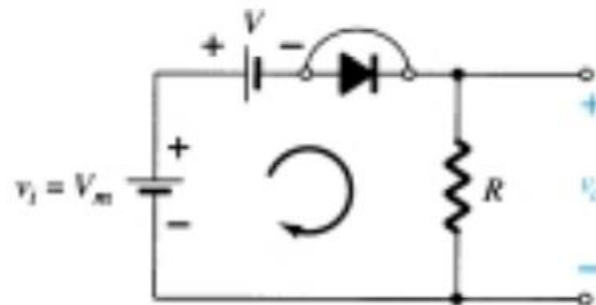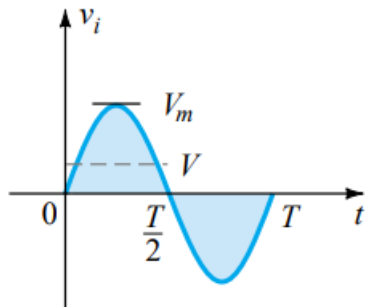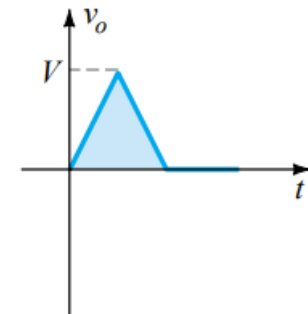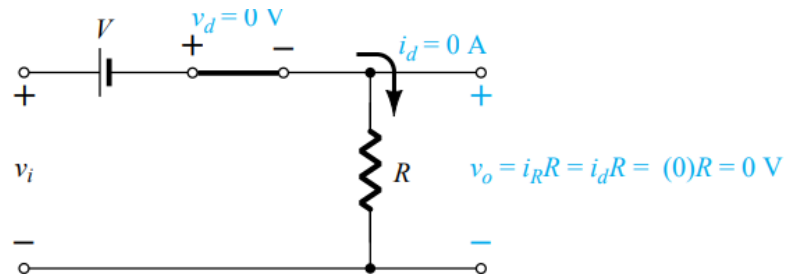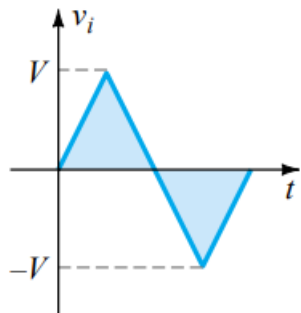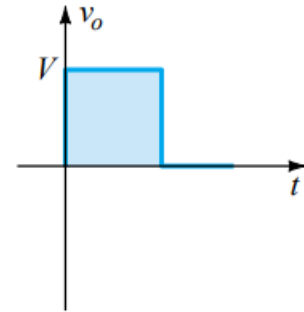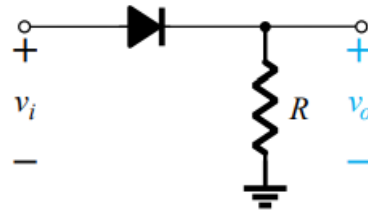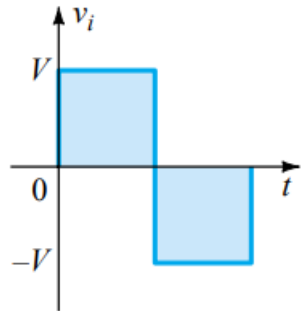

Clipper

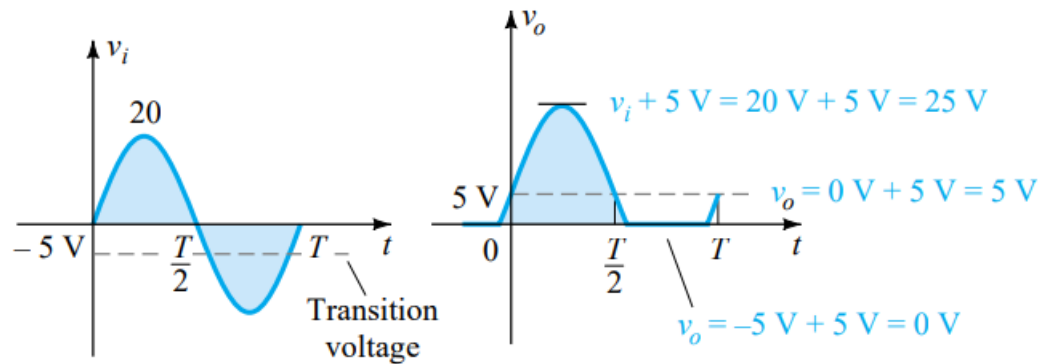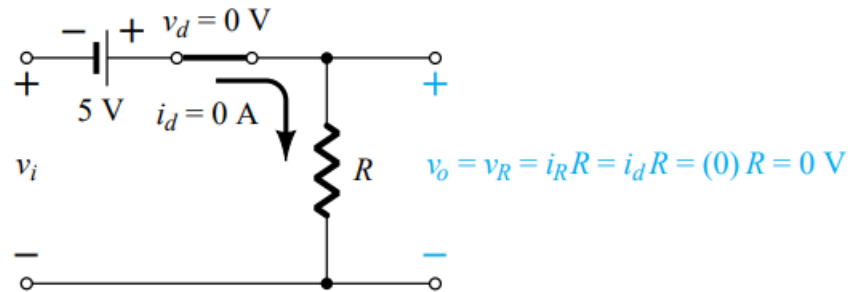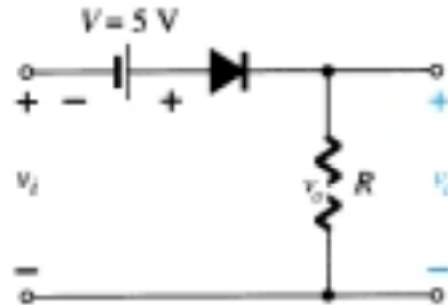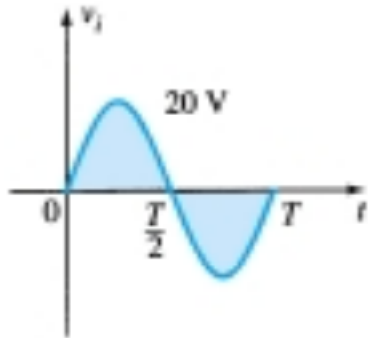

Clamper

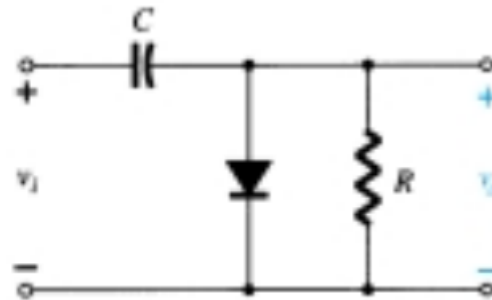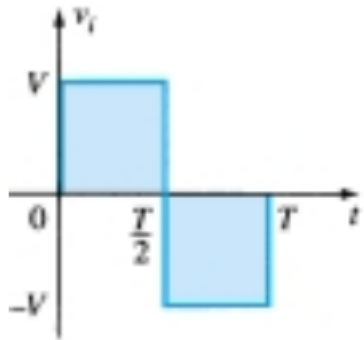

Positive Cycle:



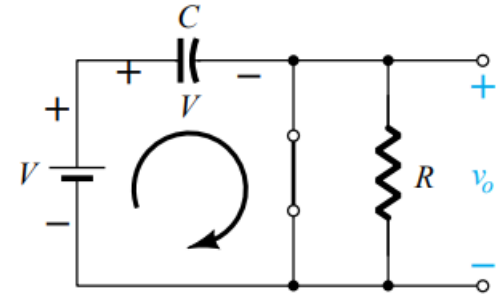









Figure 2.93 Diode “on” and the capacitor charging to V volts.

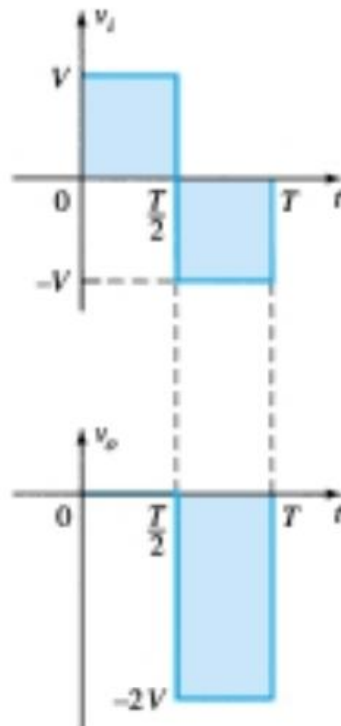

Negative Cycle:

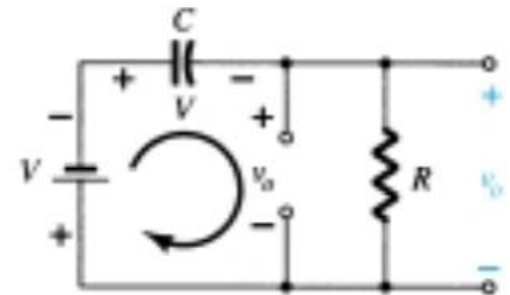

Clamper

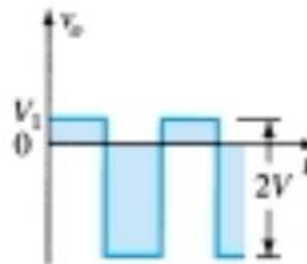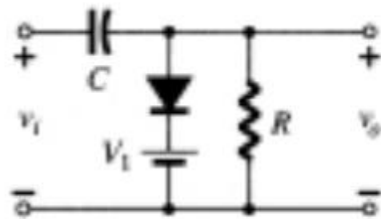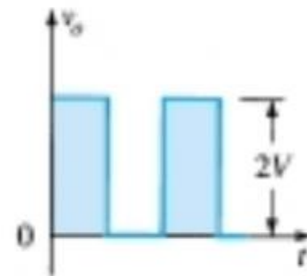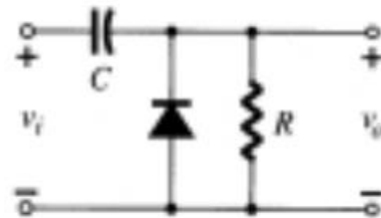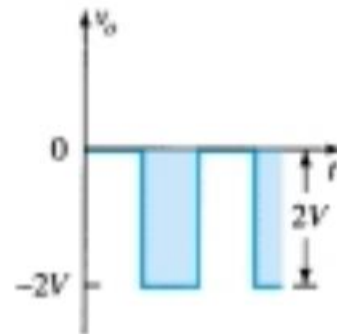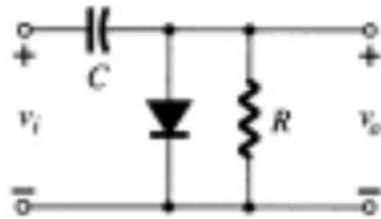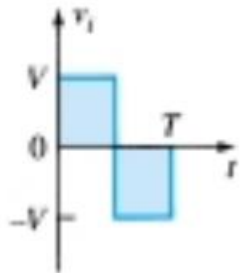

Clamper

