

# Basic Electronics Engineering (Spring 2024)

#### **Resources of PPT:**

- www.google.com
- Digital Design, 4<sup>th</sup> Edition
   M. Morris Mano and Michael D. Ciletti

## **Analog Electronics**



#### Reference Book:

- 1. R. BOYLESTAD and L. NASHELSKY, "Electronic Devices And Circuit Theory", Prentice Hall.
- 2. Sedra and Smith, "Microelectronic Circuits", Oxford University Press





# P N

Forward Bias: + -

Reverse Bias: +

 
#### **Bipolar Junction Transistor (BJT) Construction:**




 


### BJT



 

 


 
(a) NPN junction bipolar transistor with no bias voltage.



 
(b) Apply reverse bias to collector base junction.





 


 
(c) Adding forward bias to base-emitter junction



 (d) results in a small base current and large emitter and collector currents.






 


Junction type	Applied voltages	Junction bias		Mode
		B-E	B-C	Would
NPN	E < B < C	Forward	Reverse	Forward-active
	E < B > C	Forward	Forward	Saturation
	E > B < C	Reverse	Reverse	Cut-off
	E > B > C	Reverse	Forward	Reverse-active
PNP	E < B < C	Reverse	Forward	Reverse-active
	E < B > C	Reverse	Reverse	Cut-off
	E > B < C	Forward	Forward	Saturation
	E > B > C	Forward	Reverse	Forward-active

### BJT in Common Base Configuration




 

 

(a) Forward-biased junction of a *pnp* transistor.

 
(b) Reverse-biased junction of a pnp transistor




© Majority and minority carrier flow of a *pnp* transistor.

## BJT in Common Base Configuration




 

 


## BJT in Common Base Configuration



 

 
(a) Input or driving point characteristics for a common-base silicon transistor amplifier.




(b) Output or collector characteristics for a commonbase transistor amplifier.

## BJT in Common Emitter Configuration




 


 

## BJT in Common Emitter Configuration




 


 



## BJT in Common Collector Configuration



 

 


 


 


## BJT in CB, CE and CC Configuration



 

 

 

(a) Common Base (CB)

(b) Common Emitter (CE)

 $I_E = I_C + I_B$ 

$$= I_C + I_B \qquad I_C = \alpha I_E + I_{CBO}$$

$$I_C = I_{C_{\text{majority}}} + I_{CO_{\text{minority}}}$$

$$I_C = \alpha(I_C + I_B) + I_{CBO}$$

$$I_C = \frac{\alpha I_B}{1 - \alpha} + \frac{I_{CBO}}{1 - \alpha}$$

(c) Common Collector (CC)

$$\alpha_{\rm dc} = \frac{I_C}{I_E}$$

$$\alpha_{\rm ac} = \frac{\Delta I_C}{\Delta I_E} \bigg|_{V_{CB} = \text{ constant}}$$

$$\beta_{\rm dc} = \frac{I_C}{I_B}$$

$$\beta_{\rm ac} = \frac{\Delta I_C}{\Delta I_B} \bigg|_{V_{CE} = \text{ constant}}$$

## BJT Biasing



 


Fig.: Various operating points within the limits of operation of a transistor.



 


Figure 4.2 Fixed-bias circuit.



 


Figure 4.2 Fixed-bias circuit.



 


Fig.: dc equivalent circuit.

 


Fig: Base-emitter loop

$$+V_{CC}-I_BR_B-V_{BE}=0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$




 


Fig: Collector—emitter loop.

$$I_C = \beta I_B$$


$$V_{CE} = V_{CC} - I_C R_C$$

 

Determine the following

- (a)  $I_{B_Q}$  and  $I_{C_Q}$ .
- (b)  $V_{CE_Q}$ .
- (c)  $V_B$  and  $V_C$ .
- (d)  $V_{BC}$ .



 

**Figure 4.7** dc fixed-bias circuit for Example 4.1.

#### Solution

(a) Eq. (4.4): 
$$I_{B_Q} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{240 \text{ k}\Omega} = 47.08 \ \mu\text{A}$$

Eq. (4.5): 
$$I_{C_O} = \beta I_{B_O} = (50)(47.08 \ \mu\text{A}) = 2.35 \ \text{mA}$$

(b) Eq. (4.6): 
$$V_{CE_Q} = V_{CC} - I_C R_C$$
  
= 12 V - (2.35 mA)(2.2 k $\Omega$ )  
= **6.83** V

(c) 
$$V_B = V_{BE} = 0.7 \text{ V}$$
  
 $V_C = V_{CE} = 6.83 \text{ V}$ 

(d) Using double-subscript notation yields

$$V_{BC} = V_B - V_C = 0.7 \text{ V} - 6.83 \text{ V}$$
  
= -6.13 V

with the negative sign revealing that the junction is reversed-biased, as it should be for linear amplification.



#### **Load-Line Analysis**


$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CE} = V_{CC} - (0)R_C$$

$$V_{CE} = V_{CC}|_{I_C=0 \text{ mA}}$$

$$0 = V_{CC} - I_C R_C$$

$$I_C = \frac{V_{CC}}{R_C} \bigg|_{V_{cx} = 0 \text{ V}}$$

 

 


Fig: Fixed-bias load line



 


Fig: BJT bias circuit with emitter resistor.

$$+V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I_E = (\beta + 1)I_B$$

$$-I_B (R_B + (\beta + 1)R_E) + V_{CC} - V_{BE} = 0$$


 


Fig: Base-emitter loop

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$

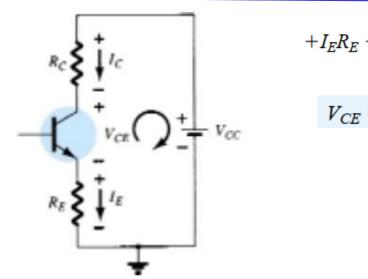Note that the only difference between this equation for  $I_B$  and that obtained for the fixed-bias configuration is the term  $(1+\beta)R_E$ .





$$+I_{E}R_{E} + V_{CE} + I_{C}R_{C} - V_{CC} = 0$$

$$I_{E} \cong I_{C}$$

$$V_{CE} = V_{CC} - I_{C}(R_{C} + R_{E})$$

$$V_{E} = I_{E}R_{E}$$

$$V_{C} = V_{CE} + V_{E}$$

$$V_{C} = V_{CC} - I_{C}R_{C}$$

$$V_B = V_{CC} - I_B R_B$$

$$V_B = V_{BE} + V_E$$

Fig: Collector-emitter loop

#### **Improved Bias Stability**

The addition of the emitter resistor to the dc bias of the BJT provides improved stability, that is, the dc bias currents and voltages remain closer to where they were set by the circuit when outside conditions, such as temperature, and transistor beta, change.



#### **Load-Line Analysis**

 


Fig: Load line for the emitter-bias configuration.


$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

$$V_{CE} = V_{CC} \big|_{I_C = 0 \text{ mA}}$$

$$I_C = \frac{V_{CC}}{R_C + R_E} \bigg|_{V_{CE} = 0 \text{ V}}$$

For the emitter bias network of Fig. 4.22, determine:

- (a)  $I_B$ .
- (b)  $I_C$ .
- (c)  $V_{CE}$ .
- (d) V<sub>C</sub>.
- (e)  $V_E$ .
- (f)  $V_B$ .
- (g)  $V_{BC}$ .

 

**Figure 4.22** Emitter-stabilized bias circuit for Example 4.4.



(a) Eq. (4.17): 
$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} = \frac{20 \text{ V} - 0.7 \text{ V}}{430 \text{ k}\Omega + (51)(1 \text{ k}\Omega)}$$
 (b)  $I_C = \beta I_B$  = (50)(40.1  $\mu$ A)  $\approx 2.01 \text{ mA}$ 

(c) Eq. (4.19): 
$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$
  
= 20 V - (2.01 mA)(2 k $\Omega$  + 1 k $\Omega$ ) = 20 V - 6.03 V  
= 13.97 V

(d) 
$$V_C = V_{CC} - I_C R_C$$
 (e)  $V_E = V_C - V_{CE}$   
= 20 V - (2.01 mA)(2 k $\Omega$ ) = 20 V - 4.02 V = 15.98 V - 13.97 V  
= **15.98** V

(f) 
$$V_B = V_{BE} + V_E$$
 (g)  $V_{BC} = V_B - V_C$   
= 0.7 V + 2.01 V = 2.71 V - 15.98 V  
= -13.27 V (reverse-biased as required)

## BJT Voltage Divider BIAS




 



Figure 4.25 Voltage-divider bias configuration.

 


**Figure 4.27** Redrawing the input side of the network of Fig. 4.25.

## BJT Voltage Divider BIAS




 

$$R_{\rm Th} = R_1 || R_2$$

 

$$E_{\rm Th} = V_{R_2} = \frac{R_2 V_{CC}}{R_1 + R_2}$$

 

**Figure 4.30** Inserting the Thévenin equivalent circuit.

$$E_{\rm Th} - I_B R_{\rm Th} - V_{BE} - I_E R_E = 0$$

$$I_E = (\beta + 1)I_B$$

$$I_B = \frac{E_{\rm Th} - V_{BE}}{R_{\rm Th} + (\beta + 1)R_E}$$


$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

## BJT Voltage Divider BIAS



$$I_C = \frac{V_{CC}}{R_C + R_E} \bigg|_{VCE} = 0 \text{ V}$$

$$V_{CE} = V_{CC}|_{I_C = 0 \text{ mA}}$$

 

**Figure 4.24** Load line for the emitter-bias configuration.

#### BJT VOLTAGE FEEDBACK BIAS



 


Fig: BJT with voltage feedback bias

$$V_{CC} - I'_C R_C - I_B R_B - V_{BE} - I_E R_E = 0$$
  
 $I'_C \cong I_C = \beta I_B \text{ and } I_E \cong I_C$ 

$$V_{CC} - \beta I_B R_C - I_B R_B - V_{BE} - \beta I_B R_E = 0$$

 


Fig: Base-emitter loop

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)}$$

### BJT VOLTAGE FEEDBACK BIAS



 


Fig: Collector-emitter loop


$$I_E R_E + V_{CE} + I'_C R_C - V_{CC} = 0$$

Since  $I'_C \cong I_C$  and  $I_E \cong I_C$ , we have

$$I_C(R_C + R_E) + V_{CE} - V_{CC} = 0$$

and  $V_{CE}$ 

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

 

Determine the quiescent levels of  $I_{C_o}$  and  $V_{CE_o}$  for the network

$$I_{B} = \frac{V_{CC} - V_{BE}}{R_{B} + \beta(R_{C} + R_{E})}$$

$$= \frac{10 \text{ V} - 0.7 \text{ V}}{250 \text{ k}\Omega + (90)(4.7 \text{ k}\Omega + 1.2 \text{ k}\Omega)}$$

$$= \frac{9.3 \text{ V}}{250 \text{ k}\Omega + 531 \text{ k}\Omega} = \frac{9.3 \text{ V}}{781 \text{ k}\Omega}$$

$$= 11.91 \mu\text{A}$$

$$V_{CE_{Q}} = V_{CC} - I_{C}(R_{C} + R_{E})$$

$$= 10 \text{ V} - (1.07 \text{ mA})(4.7 \text{ k}\Omega + 1.2 \text{ k}\Omega)$$

$$= 10 \text{ V} - 6.31 \text{ V}$$

$$= 3.69 \text{ V}$$

## BJT Stability Analysis



#### Stability Factors, $S(I_{CO})$ , $S(V_{BE})$ , and $S(\beta)$

$$S(I_{CO}) = \frac{\Delta I_C}{\Delta I_{CO}}$$

$$S(V_{BE}) = \frac{\Delta I_C}{\Delta V_{BE}}$$

$$S(\beta) = \frac{\Delta I_C}{\Delta \beta}$$

#### $S(I_{CO})$ : EMITTER-BIAS CONFIGURATION

For the emitter-bias configuration, an analysis of the network will result in

$$S(I_{CO}) = (\beta + 1) \frac{1 + R_B/R_E}{(\beta + 1) + R_B/R_E}$$

For the fixed-bias configuration,

$$S(I_{CO}) = \beta + 1$$

#### **Voltage-Divider Bias Configuration**

$$S(I_{CO}) = (\beta + 1) \frac{1 + R_{Th}/R_E}{(\beta + 1) + R_{Th}/R_E}$$


#### Feedback-Bias Configuration


$$S(I_{CO}) = (\beta + 1) \frac{1 + R_B/R_C}{(\beta + 1) + R_B/R_C}$$
 
### BJT AS SWITCHING CIRCUIT



A BJT can be used as a switching device in logic circuits to turn on or off current to a load. As a switch, the transistor is normally in either cutoff (load is OFF) or saturation (load is ON).



 


Switches between cut-off and saturation region.
 
#### **MOSFET**



MOSFET (*m*etal-*o*xide-*s*emiconductor-*f*ield-*e*ffect *t*ransistor) has four components:

- Source (S)
- > Drain (D)
- Gate (G)
- Body (B) terminals



The body (B) is frequently connected to the source terminal, reducing the terminals to three. It works by varying the width of a channel along which charge carriers flow (electrons or holes).

The charge carriers enter the channel at the source and exit via the drain. The width of the channel is controlled by the voltage on an electrode called Gate which is located between the source and the drain. It is insulated from the channel near an extremely thin layer of metal oxide.


- □ Depletion Type − the transistor requires the Gate-Source voltage, (V<sub>GS</sub>) to switch the device "OFF". The depletion mode MOSFET is equivalent to a "Normally Closed" switch.
- □ Enhancement Type − the transistor requires a Gate-Source voltage, (V<sub>GS</sub>) to switch the device "ON". The enhancement mode MOSFET is equivalent to a "Normally Open" switch.

### **MOSFET**





#### There are four types of MOSFET:

 - 1. P-Channel Depletion MOSFET
- 2. P-Channel Enhancement MOSFET
- 3. N-Channel Depletion MOSFET
- 4. N-Channel Enhancement MOSFET Drain (D)




(a) P-Channel Depletion MOSFET

 

 

(b) P-Channel Enhancement MOSFET

 

(a) N-Channel Depletion MOSFET

(b) N-Channel Enhancement MOSFET

## N-Channel Depletion MOSFET



 


Fig: n-Channel depletion-type MOSFET with  $V_{GS} = 0$  V and an applied voltage  $V_{DD}$ 


 


Fig: Drain and transfer characteristics for an n-channel depletion-type MOSFET

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

## P-Channel Depletion MOSFET

 





p-Channel depletion-type MOSFET with  $I_{DSS} = 6$  mA and  $V_P = +6$  V.

### N-Channel Enhancement MOSFET



 

 


**Figure 5.34** Drain characteristics of an *n*-channel enhancement-type MOSFET with  $V_T = 2$  V and  $k = 0.278 \times 10^{-3}$  A/V<sup>2</sup>.

$$V_{DG} = V_{DS} - V_{GS}$$
  $V_{DS_{\text{sat}}} = V_{GS} - V_{T}$ 

$$I_D = k(V_{GS} - V_T)^2$$

### P-Channel Enhancement MOSFET




 

p-Channel enhancement-type MOSFET with  $V_T = 2 \text{ V}$  and  $k = 0.5 \times 10^{-3} \text{ A/V}^2$ .
 
## N-Channel Enhancement MOSFET as Amplifier





- 1. Cut-off Region with  $V_{GS} < V_{threshold}$  the gate-source voltage is much lower than the transistors threshold voltage so the MOSFET transistor is switched "fully-OFF" thus,  $I_D = 0$ , with the transistor acting like an open switch regardless of the value of  $V_{DS}$ .
- 2. Linear (Ohmic) Region with  $V_{GS} > V_{threshold}$  and  $V_{DS} < V_{GS}$  the transistor is in its constant resistance region behaving as a voltage-controlled resistance whose resistive value is determined by the gate voltage,  $V_{GS}$  level.
- 3. Saturation Region with  $V_{GS} > V_{threshold}$  and  $V_{DS} > V_{GS}$  the transistor is in its constant current region and is therefore "fully-ON". The Drain current  $I_D$  = Maximum with the transistor acting as a closed switch.